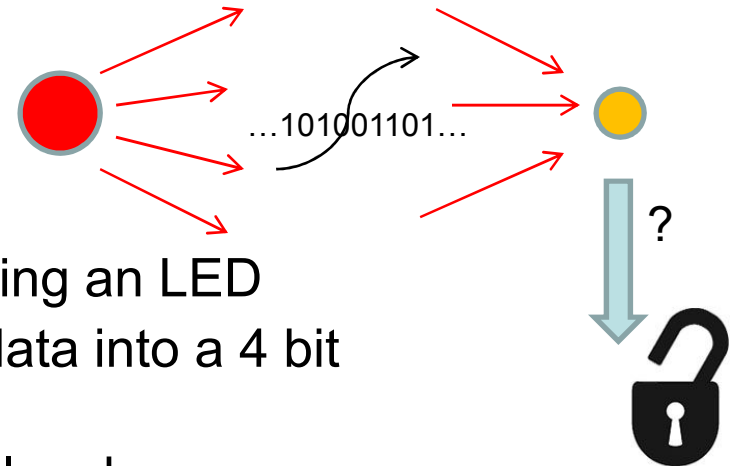



# Project: security lock system



- Idea:
  - Create a 4bit password using switches
  - Send data serially (one bit at a time) using an LED
  - Receive the code serially and convert data into a 4 bit number
  - Compare the received data with original code
  - Unlock the key if it matches!
- Potential uses: TV/ DVD/Car unlock ... remote control
- Components:
  - Timer                      -- Switch
  - Shift Register            -- Comparators
  - Amplifier
- Optional: extending the system into 8-bit

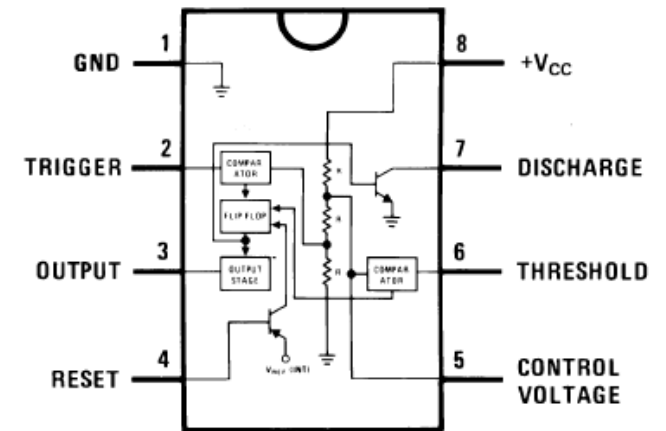
# LM555 Timer

- Used as an oscillator to drive a speaker
- **Trigger:** when  $< \frac{1}{3} V_{CC}$ , the output is high ( $V_{CC}$ )
- **Threshold input:** when  $> \frac{2}{3} V_{CC}$  and the trigger is  $> \frac{1}{3} V_{CC}$ , the output is low (0V). If the trigger is  $< \frac{1}{3} V_{CC}$ , it overrides the threshold input and holds the output high.
- **Reset input:** when less than about 0.7V, all other inputs are overridden and the output is low.
- **Discharge pin:** This is connected to 0V when the timer output is low and is used to discharge the timing capacitor in astable operation.


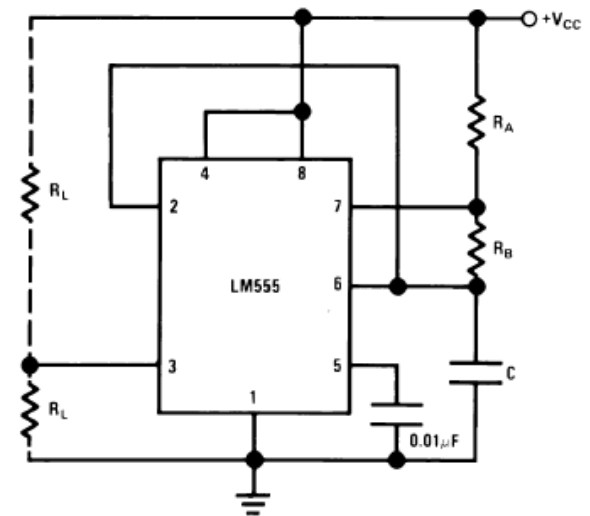
# LM555 Timer as an oscillator

- Astable operation: The circuit oscillates on its own.
- With the output high, the capacitor C is charged by current flowing through  $R_A$  and  $R_B$ .
- The threshold and trigger inputs monitor the capacitor voltage and when it reaches  $\frac{2}{3}V_{CC}$  (threshold), the output becomes low and the discharge pin is connected to 0V.
- The capacitor discharges with current flowing through  $R_B$  into the discharge pin. When the voltage falls to  $\frac{1}{3}V_{CC}$  (trigger) the output becomes high again and the discharge pin is disconnected, allowing the capacitor to start charging again.
- Adjust duty cycle (time on : total time) by adjusting the ratio between  $R_A$  and  $R_B$ .
- Note that pin 4 (reset) is held at  $V_{CC}$  here. You will need change the connection for light sensitivity.



From <http://www.national.com/ds/LM/LM555.pdf>

# LM555 Timer

- Some equations for astable operation:

The charge time (output high) is given by:

$$t_1 = 0.693 (R_A + R_B) C$$

And the discharge time (output low) by:

$$t_2 = 0.693 (R_B) C$$

Thus the total period is:


$$T = t_1 + t_2 = 0.693 (R_A + 2R_B) C$$

The frequency of oscillation is:

$$f = 1/T = 1.44 / (R_A + 2R_B) C$$


And the duty cycle is:
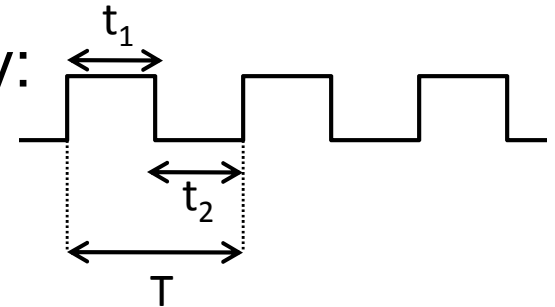
$$D = t_1 / (t_1 + t_2) = (R_A + R_B) / (R_A + 2R_B)$$


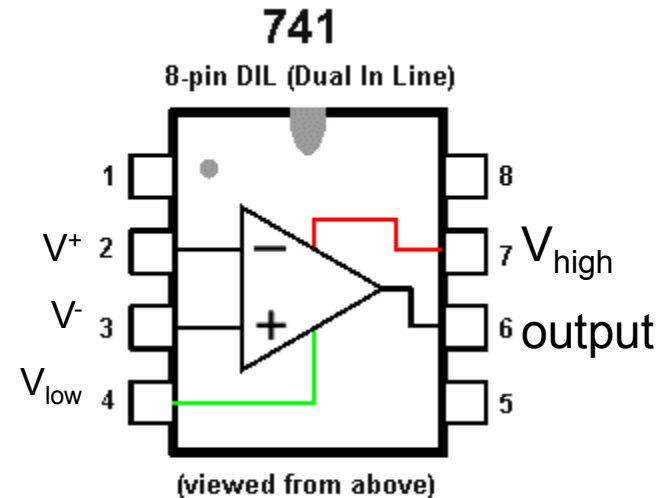
# Comparator


- Built using an op-amp (a 741 will do)
- Compares its “+” and “-” inputs
  - If  $V^+ > V^-$  then output =  $V_{\text{High}}$  (a digital “1”)
  - If  $V^+ < V^-$  then output =  $V_{\text{Low}}$  (a digital “0”)
- Useful for converting small analog voltages into big, digital signals
- To power up, attach  $V_{\text{Low}}$  to -6V,  $V_{\text{High}}$  to +6V



- Test: attach output to LED in series with a 1k $\Omega$  resistor to ground
- Set  $V^+$ ,  $V^-$  with SMUs, confirm that LED turns on when  $V^+ > V^-$
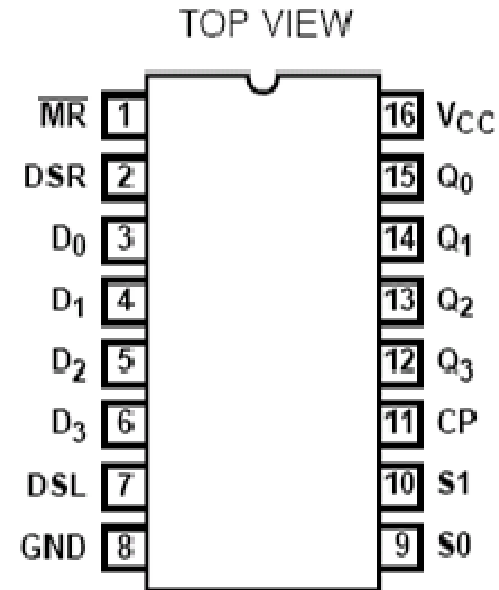
# Shift register (1)

- A shift register is a kind of digital memory
- It has 6 data inputs:
  - Parallel data D0,D1,D2,D3
  - Serial data DSR, DSL
- It has three controls:
  - Shift controls, S0, S1
  - Clock
- It has 4 outputs:
  - Q0,Q1,Q2,Q3
  - These outputs change only when the clock changes from 0 to 1



Set VCC to 5V, VSS to 0V, pin 1 to 5V


# Shift register (2)

- The shift register has 4 modes, set by S0, S1, and triggered by the clock
- When S0=1, S1 =1,
  - Q0 = D0, Q1 = D1, etc
- When S0 = 0, S1 = 0
  - Q0,Q1,Q2,Q3 hold their value
- When S0 = 0, S1 = 1
  - Data shifts left: Q1 = Q0 (from before clock) Q2= Q1, etc
  - Q0 = DSR
- When S0 = 1, S1 = 0
  - Data shifts right: Q2 = Q3 (from before clock) Q1= Q2, etc
  - Q3 = DSL
- Test:
  - attach outputs to 4 LEDs in series with 1k $\Omega$  resistors to ground
  - Set function generator to make a 5V square wave (2.5V offset) with frequency = 1Hz, attach it to the clock input
  - Short D0, D2, D3, SDR to ground, short D1, SDL to 5V
- Try different combinations of S0, S1.
- What happens?
  - You should see things shift left or right.

# Comparator (1)


- Includes combination of AND and XOR gated:

- AND:

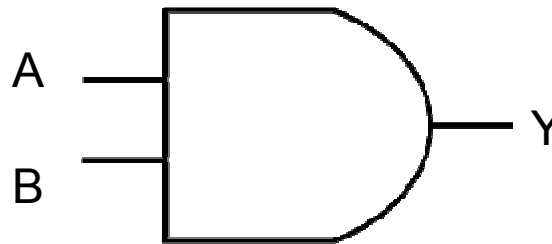


Y=1 if A=B=1,  
otherwise Y=0

- XOR:

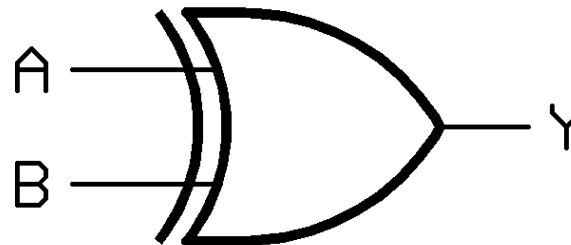


False if A=B  
True if A≠B

- NOT

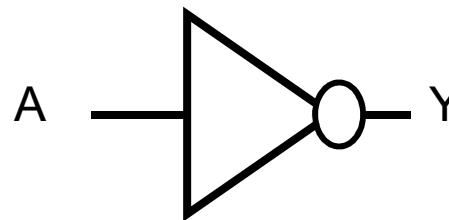


If A=1, Y=0, if A=0, Y=1

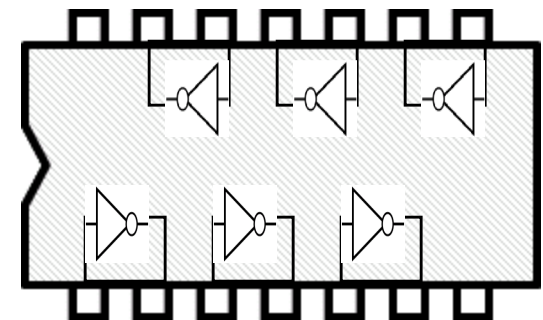

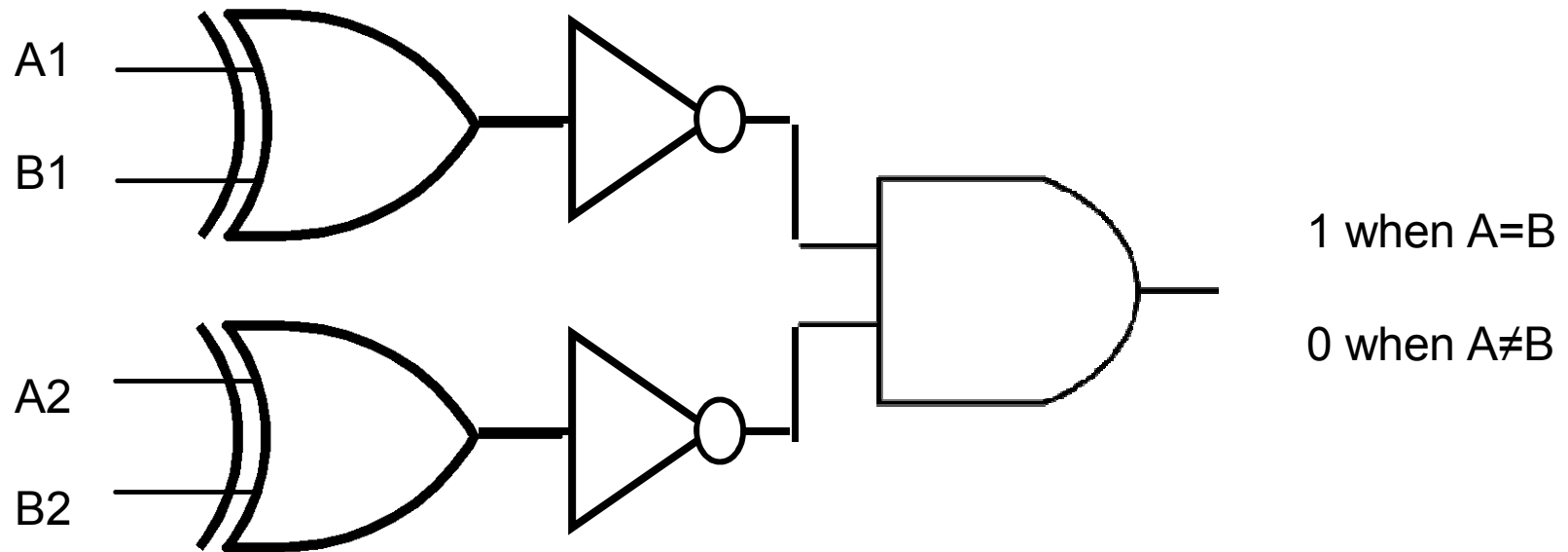
# Comparator (2)

- Comparing two 2-bit numbers:  $A = A_2, A_1$   
 $B = B_2, B_1$



# Latch circuit

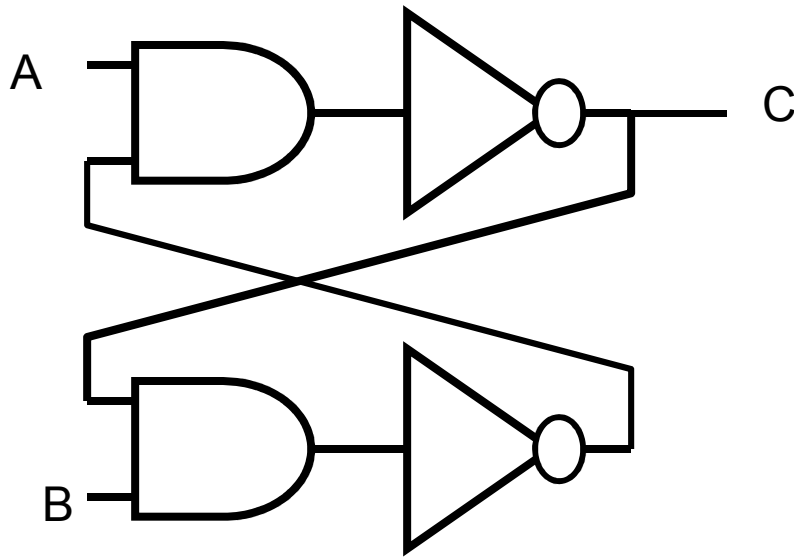

Question: write a truth table for this circuit: what happens when  $A=B=1$ ?

Test: hook up and gates as you did yesterday, test its function: does it behave as you predicted?