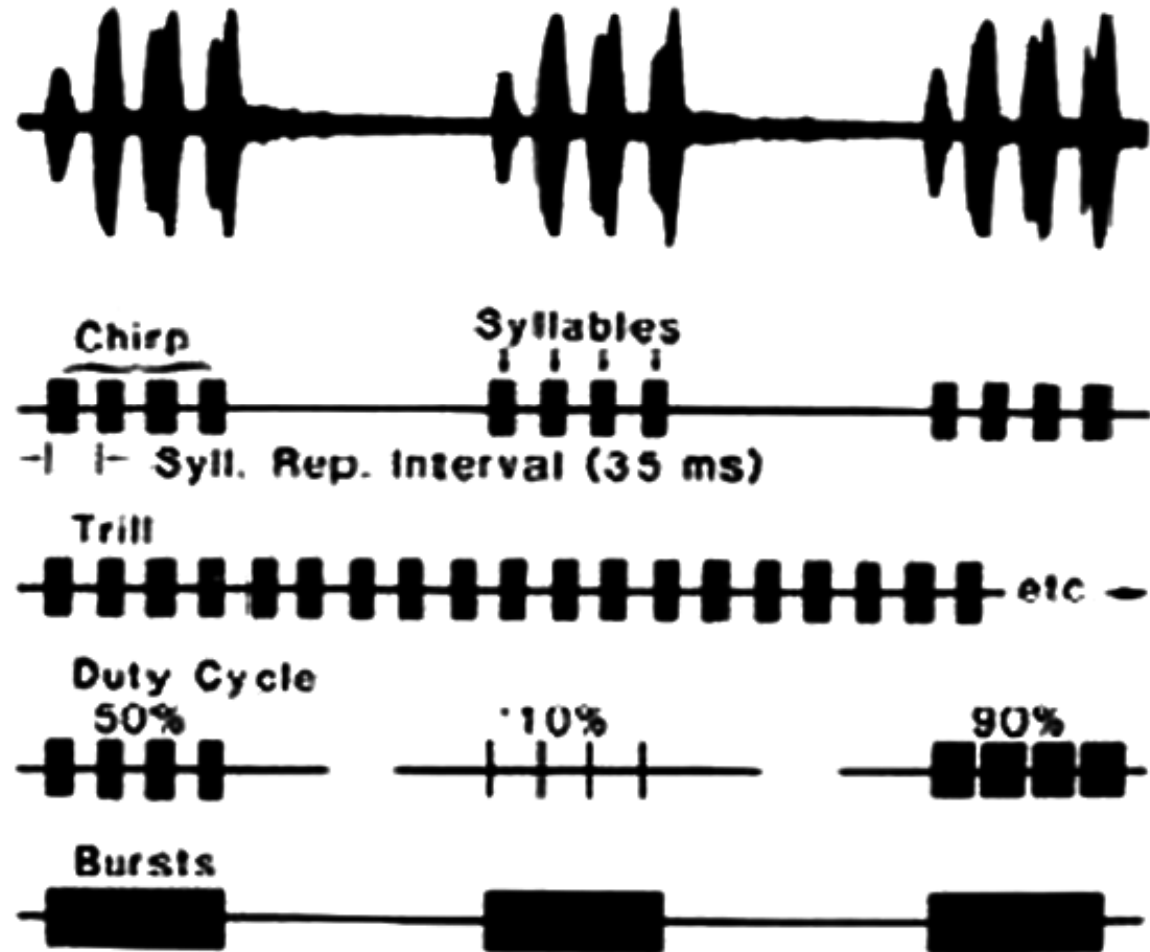


Project: Electronic Cricket

- Idea:
 - Use photoresistor to detect light, only chirp when dark
 - Create sort-of-realistic cricket noise using several oscillators
 - Match to real cricket calls: google “cricket chirping”
- Potential uses: annoy people; investigate cricket social interactions (see Genetic Control of Acoustic Behavior in Crickets – Ron Hoy)
- Components:
 - Photoresistor
 - Oscillators
 - Speaker

Structure of a Cricket Call


- Field cricket:
- Syll. frequency 4-5 kHz.
- Syll. Repeat 35 mSec
- Duty Cycle ~50%
- Chirp repeat rate ~2-4/sec



From <http://www.uni-graz.at/~hartbaue/introduction.html>


LM555 Timer

- Used as an oscillator to drive a speaker
- **Trigger:** when $< \frac{1}{3} V_{cc}$, the output is high (V_{cc})
- **Threshold input:** when $> \frac{2}{3} V_{cc}$ and the trigger is $> \frac{1}{3} V_{cc}$, the output is low (0V). If the trigger is $< \frac{1}{3} V_{cc}$, it overrides the threshold input and holds the output high.
- **Reset input:** when less than about 0.7V, all other inputs are overridden and the output is low.
- **Discharge pin:** This is connected to 0V when the timer output is low and is used to discharge the timing capacitor in astable operation.

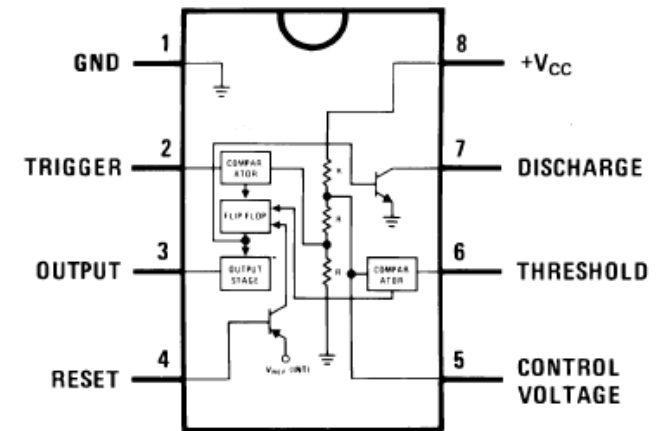

LM555 Timer as an oscillator

- Astable operation: The circuit oscillates on its own.
- With the output high, the capacitor C is charged by current flowing through R_A and R_B .
- The threshold and trigger inputs monitor the capacitor voltage and when it reaches $\frac{2}{3}V_{cc}$ (threshold), the output becomes low and the discharge pin is connected to 0V.
- The capacitor discharges with current flowing through R_B into the discharge pin. When the voltage falls to $\frac{1}{3}V_{cc}$ (trigger) the output becomes high again and the discharge pin is disconnected, allowing the capacitor to start charging again.
- Adjust duty cycle (time on : total time) by adjusting the ratio between R_A and R_B .
- Note that pin 4 (reset) is held at V_{cc} here. You will need change the connection for light sensitivity.

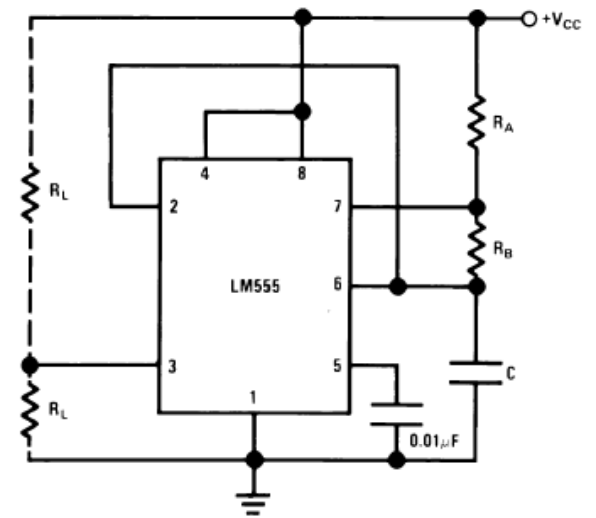

From <http://www.national.com/ds/LM/LM555.pdf>

LM555 Timer

- Some equations for astable operation:

The charge time (output high) is given by:

$$t_1 = 0.693 (R_A + R_B) C$$

And the discharge time (output low) by:

$$t_2 = 0.693 (R_B) C$$

Thus the total period is:


$$T = t_1 + t_2 = 0.693 (R_A + 2R_B) C$$

The frequency of oscillation is:

$$f = 1/T = 1.44 / (R_A + 2R_B) C$$


And the duty cycle is:

$$D = t_1 / (t_1 + t_2) = (R_A + R_B) / (R_A + 2R_B)$$

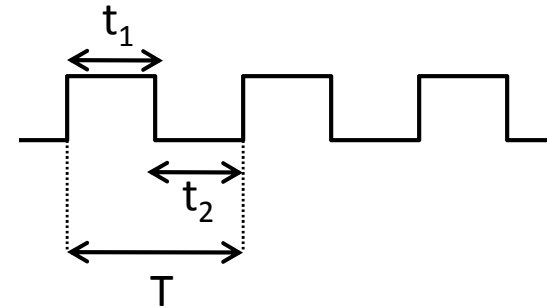

LM555

- Testing:
 - Pick a large-ish capacitor (say $10\mu\text{F}$), and a few different resistors ($1\text{k}\Omega$, $10\text{k}\Omega$, $51\text{k}\Omega$, $100\text{k}\Omega$, etc...) or a couple of 10 or $100\text{k}\Omega$ potentiometers (variable resistors)
 - Build the circuit to the right *without* the speaker
 - Probe the output with the oscilloscope (Do you see a square wave?)
 - Try different resistors
 - What happens to the frequency?
 - What happens to the duty cycle?

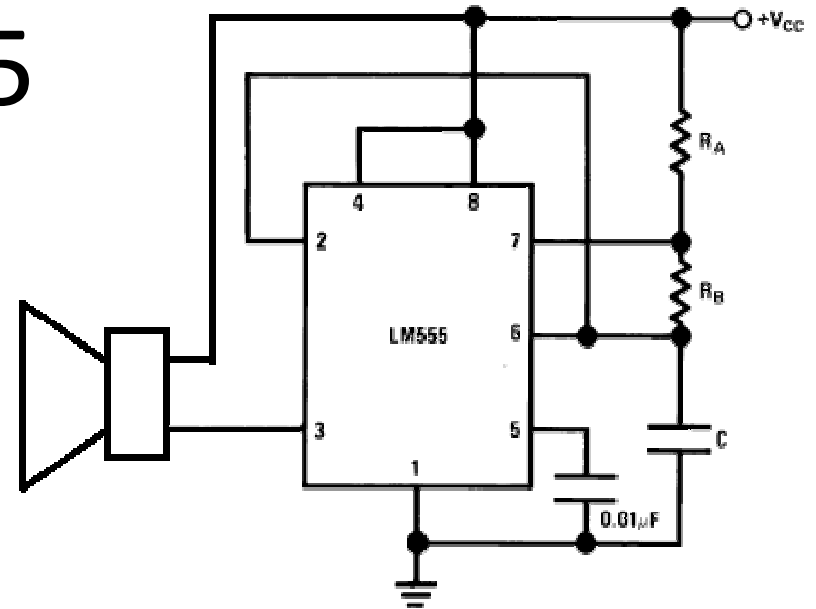

- Next, add the speaker
- Can you hear anything? Adjust the resistors (or cap) until you do
- CHALLENGE: Achieve a $<50\%$ duty cycle
 - Hint: you might need an additional component

Photoresistor

- Photoresistor Testing:
 - Use the Ohm meter to measure the resistance of the photoresistor.
 - Shine light on the photoresistor. What happens to the resistance?
 - What is the resistance range going from room light to complete darkness?
 - The 555 timer turns on if the voltage at pin 4 is greater than 1 volt. Build a voltage divider to connect to pin 4 which goes above 1 volt in the dark.